

**Project Title: Finite State Device**

**Course: ELET 1210 – DIGITAL EELECTRONICS 1**

**Author: Nickeem Payne-Deacon**

**Contact Details: [nickeem.payne-deacon@mycavehill.uwi.edu](mailto:nickeem.payne-deacon@mycavehill.uwi.edu)**

## Contents

Introduction .....	3
Description of Experimental Setup/List of Equipment Used.....	3
Logic Diagram.....	4
Pictorial Diagram.....	4
State Diagram.....	5
Procedure/Method .....	5
Results.....	6
Discussion and Conclusion .....	8

## Introduction

This report will be discussing Flip Flops, specifically a J-K Flip Flop. Flip flops are the most basic memory devices used for information storage in sequential circuits. There are 1-bit memory devices where the output depends not only on the present value of the input, but the previous value as well. In this lab a synchronous finite state device will be designed based on a sequence using a J-K flip flop. The J-K flip flop device will then be analysed through tables, diagrams, and circuits to check and verify it cycles through its sequence correctly and is self-correcting.

## Description of Experimental Setup/List of Equipment Used


The equipment used for this experiment include, a power supply, DIP switch, 2 breadboards, wires, resistors, push button, 7 segment display and ICs.

Required IC's:

74HC73 Dual J-K Flip Flop – 2

74HC32 Quad 2 – Input OR

### Pictorial Diagram

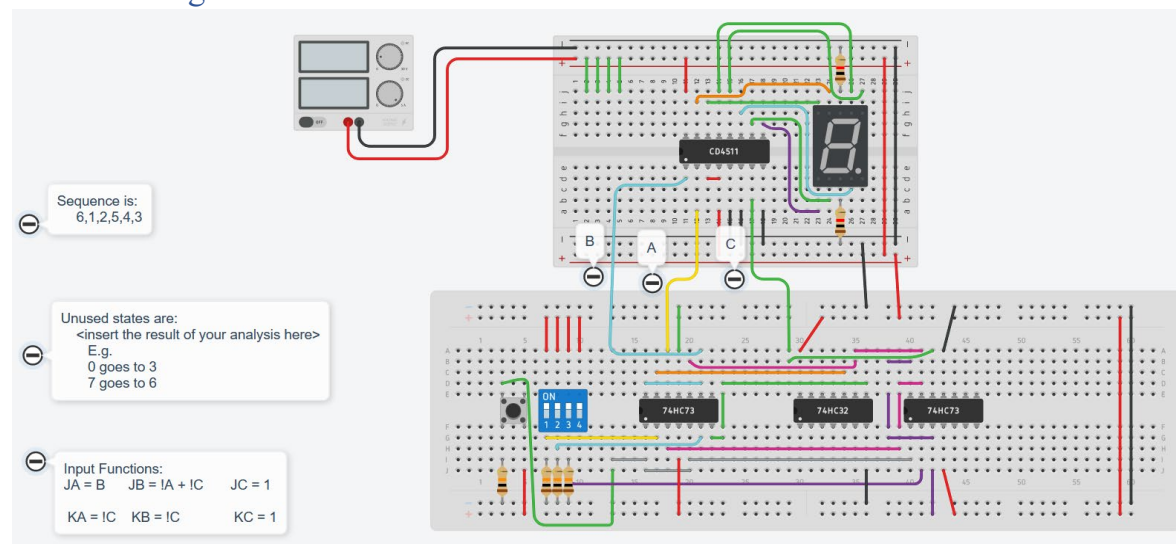

IC Positions: 1- 73HC73, 2- OR 3-73HC73

## State Diagram

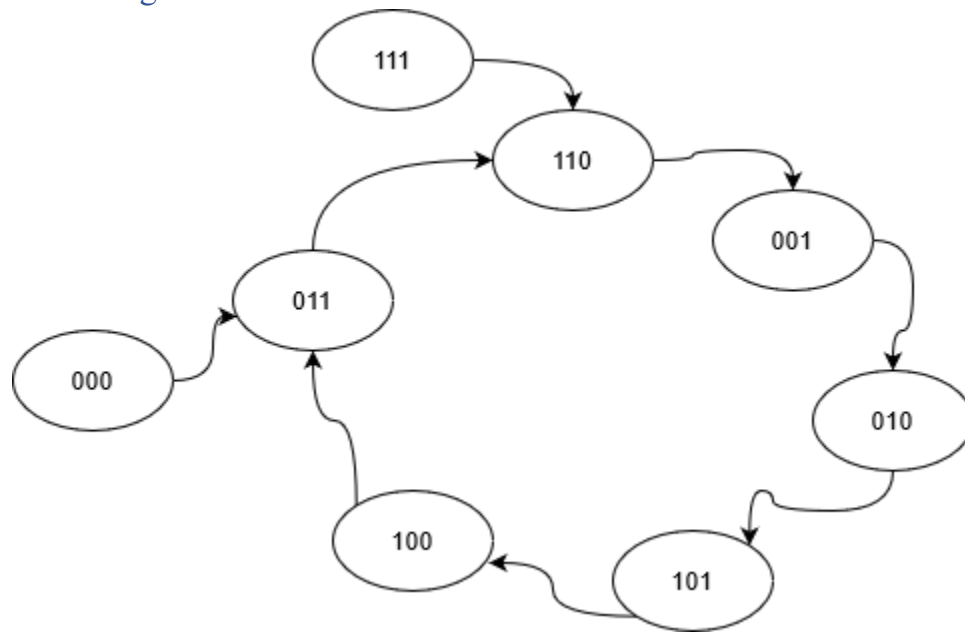


Figure C: State Diagram of Finite State Device using J-K Flip Flop

## Procedure/Method

A count sequence was given and used to produce tables D-K. The input functions resulting from the tables were then used to create the diagrams from Figure A and C. The circuit template was used and then implemented based on the input functions calculated and IC positions given. The circuit was set up as shown in figure B. The device was tested by turning on the power supply, setting the inputs on the DIP switch to on and the pushbutton was pressed to cycle through numbers in a sequence that was displayed on the 7-segment display. After different inputs were checked and the sequence was verified the power supply was turned off.

## Results

Sequence – 6,1,2,5,4,3

Type of flip Flop = J-K

State Table													
Present State				Next State			Flip Flop Functions						
sequence	A	B	C	A	B	C	$J_A$	$K_A$	$J_B$	$K_B$	$J_C$	$K_C$	
6	1	1	0	0	0	1	X	1	X	1	1	X	
1	0	0	1	0	1	0	0	X	1	X	X	1	
2	0	1	0	1	0	1	1	X	X	1	1	X	
5	1	0	1	1	0	0	X	0	0	X	X	1	
4	1	0	0	0	1	1	X	1	1	X	1	X	
3	0	1	1	1	1	0	1	X	X	0	X	1	

Figure D

Simplify the function of each input:

		00		01		11		10	
BC A									
		0	1	3	2	4	5	7	6
0		X	0	1	1				
1		X	X	X	X				

Present State				Flip Flop Function
	A	B	C	$J_A$
6	1	1	0	X
1	0	0	1	0
2	0	1	0	1
5	1	0	1	X
4	1	0	0	X
3	0	1	1	1

$$J_A = B$$

Figure E

		00		01		11		10	
BC A									
		0	1	3	2	4	5	7	6
0		X	X	X	X				
1		1	0	X	1				

Present State				Flip Flop Function
	A	B	C	$K_A$
6	1	1	0	1
1	0	0	1	X
2	0	1	0	X
5	1	0	1	0
4	1	0	0	1
3	0	1	1	X

$$K_A = \overline{C}$$

Figure F

		00		01		11		10	
BC A		0		1		3		2	
		0	X	1	1	X	X	X	X
1		4	1	5	0	7	X	6	X

$$J_B = \bar{A} + \bar{C}$$

Present State				Flip Flop Function	
	A	B	C		$J_B$
6	1	1	0		X
1	0	0	1		1
2	0	1	0		X
5	1	0	1		0
4	1	0	0		1
3	0	1	1		X

Figure G

		00		01		11		10	
BC A		0		1		3		2	
		0	X	X	X	0	1	1	1
1		4	X	X	X	7	X	6	1

Present State				Flip Flop Function	
	A	B	C		$K_B$
6	1	1	0		1
1	0	0	1		X
2	0	1	0		1
5	1	0	1		X
4	1	0	0		X
3	0	1	1		0

$$K_B = \bar{C}$$

Figure H

		00		01		11		10	
BC A		0		1		3		2	
		0	X	X	X	X	1	1	1
1		4	1	X	X	7	X	6	1

Present State				Flip Flop Function	
	A	B	C		$J_C$
6	1	1	0		1
1	0	0	1		X
2	0	1	0		1
5	1	0	1		X
4	1	0	0		1
3	0	1	1		X

$$J_C = 1$$

Figure I

		00		01		11		10	
BC A		0		1		3		2	
		0	X	1	1	1	X	X	X
1		4	X	1	X	7	X	6	X

Present State				Flip Flop Function	
	A	B	C		$K_C$
6	1	1	0		X
1	0	0	1		1
2	0	1	0		X
5	1	0	1		1
4	1	0	0		X
3	0	1	1		1

$$K_C = 1$$

Figure J

### Input Functions

$$J_A = B \quad J_B = \overline{A} + \overline{C} \quad J_C = 1$$

$$K_A = \overline{C} \quad K_B = \overline{C} \quad K_C = 1$$

### Analyzing unused state

Present State										Next State		
	A	B	C	$J_A$	$K_A$	$J_B$	$K_B$	$J_C$	$K_C$	A	B	C
0	0	0	0	0	1	1	1	1	1	0	1	1
7	1	1	1	1	0	0	0	1	1	1	1	0

Figure K

## Discussion and Conclusion

To conclude, nothing unusual was shown and results were shown as expected. A synchronous finite state device using J-K Flip Flops was designed based on a given sequence and implemented. The sequence was used to show the state table, input functions, state diagram and logic diagram and then proved to work through a circuit. The circuit proved the device sequence cycled correctly and showed it was self-correcting.